

ADVENT TERM 2 – CYCLE A
SCIENCE – Year 6 and Year 5 - Medium Term Planning – PHYSICS: ELECTRICITY

<u>LESSON 1</u>	<u>LESSON 2</u>	<u>LESSON 3</u>
Recap & retrieval: <ul style="list-style-type: none"> Electricity is a form of energy that makes things work. (Recap on Y4 Electricity) 	Recall & retrieval: <ul style="list-style-type: none"> There are recognised symbols for different components of circuits. 	Recall & retrieval: <ul style="list-style-type: none"> There are recognised symbols for different components of circuits. A collection of components connected by wires in a loop is called a series circuit.
LEARNING INTENTION: Year 5 To know that a circuit is made up of different components. (Y4 recap). To know that there are recognised symbols for different components of circuits. Year 6 To know that a circuit is made up of different components. (Y4 recap). To know and explain the recognised symbols for different components of circuits. Skills: Disciplinary Knowledge: Year 5 <ul style="list-style-type: none"> Use recognised symbols when representing a simple circuit in a diagram. (support) Year 6 <ul style="list-style-type: none"> Use recognised symbols when representing a simple circuit in a diagram. Aim: Develop scientific knowledge and conceptual understanding through the specific disciplines of physics.	LEARNING INTENTION: Year 5 To know that series circuits can be recorded using recognised symbols for different components. Year 6 To know and understand that series circuits can be recorded using recognised symbols for different components. Skills: Disciplinary Knowledge: Year 5 <ul style="list-style-type: none"> Use recognised symbols when representing a simple circuit in a diagram. (support) Year 6 <ul style="list-style-type: none"> Use recognised symbols when representing a simple circuit in a diagram. Aim: Develop scientific knowledge and conceptual understanding through the specific disciplines of physics.	Observing and Measuring LEARNING INTENTION: Year 5 To know that the volume of a buzzer will change when the wire length is altered. Year 6 To know and explain that the volume of a buzzer will change when the wire length is altered. Skills: Disciplinary Knowledge: Year 5 <ul style="list-style-type: none"> Take measurements, using a range of scientific equipment, with increasing accuracy and precision. Year 6 <ul style="list-style-type: none"> Take measurements, using a range of scientific equipment, with increasing accuracy and precision, taking repeat readings when appropriate Aim: Develop understanding of the nature, processes and methods of science through different types of science enquiries that help them to answer scientific questions about the world around them.
Key Vocabulary: materials, electrical conductors, electrical insulators, flow, symbol, component, cell, lamp, motor, open switch, closed switch, wire, buzzer, LED, battery, voltmeter	Key Vocabulary: symbol, component, cell, lamp, motor, open switch, closed switch, wire, buzzer, LED, battery, voltmeter, series circuit	Key Vocabulary: wire, resistance, volume, buzzer, sound quality, circuit, length
Key Knowledge:	Key Knowledge:	Key Knowledge:

<p>Child:</p> <ul style="list-style-type: none"> Materials that allow electricity to flow through them are called electrical conductors. Materials that do not allow electricity to flow through them are called electrical insulators. There are recognised symbols for different components of circuits. <p>Teacher:</p> <ul style="list-style-type: none"> Electricity is a form of energy that makes things work. (Y4 Recap) Circuit components include cells, buzzers, switches, wires, lamps and motors. 	<p>Child:</p> <ul style="list-style-type: none"> A collection of components connected by wires in a loop is called a series circuit. When electricity flows through all the components of a circuit, it is called a complete circuit. When electricity cannot flow through all the components of a circuit, it is called an incomplete circuit. Symbols allow for universal identification. <p>Teacher:</p> <ul style="list-style-type: none"> Circuit symbols are used in circuit diagrams showing how a circuit is connected together. A circuit diagram is a simplified drawing that represents a real electrical circuit. 	<p>Child:</p> <ul style="list-style-type: none"> The greater the length of wire, the greater the resistance. The greater the resistance, the lesser the volume. <p>Teacher:</p> <ul style="list-style-type: none"> Resistance measures how well a material or object conducts electricity. Low resistance means the object conducts electricity well. High resistance means the object does not conduct electricity well.
---	---	--

ADVENT TERM 2 – CYCLE A
SCIENCE – Year 6 and Year 5 - Medium Term Planning – PHYSICS: ELECTRICITY

<u>LESSON 4</u>	<u>LESSON 5</u>	<u>LESSON 6</u>
Recall & retrieval: <ul style="list-style-type: none"> There are recognised symbols for different components of circuits. A collection of components connected by wires in a loop is called a series circuit. The greater the resistance, the lesser the volume. 	Recall & retrieval: <ul style="list-style-type: none"> There are recognised symbols for different components of circuits. A collection of components connected by wires in a loop is called a series circuit. The greater the resistance, the lesser the volume. When a switch is closed, it completes the circuit and allows a current to flow all the way around it. 	Recall & retrieval: <ul style="list-style-type: none"> There are recognised symbols for different components of circuits. A collection of components connected by wires in a loop is called a series circuit. The greater the resistance, the lesser the volume. When a switch is closed, it completes the circuit and allows a current to flow all the way around it. The higher the current, the higher the brightness.
Using Scientific Evidence LEARNING INTENTION: Year 5 To know that a switch can open and close a series circuit. Year 6 To know, show and explain that a switch can open and close a series circuit. Skills: Disciplinary Knowledge: Year 5 <ul style="list-style-type: none"> Identify scientific evidence that has been used to support or refute ideas. Year 6 <ul style="list-style-type: none"> Identify scientific evidence that has been used to support or refute ideas or arguments. Aim: Develop understanding of the nature, processes and methods of science through different types of science enquiries that help them to answer scientific questions about the world around them.	Observing and Measuring LEARNING INTENTION: Year 5 To know that the voltage of a cell in a circuit affects the brightness of a lamp. Year 6 To know and explain that the voltage of a cell in a circuit affects the brightness of a lamp. Skills: Disciplinary Knowledge: Year 5 <ul style="list-style-type: none"> Take measurements, using a range of scientific equipment, with increasing accuracy and precision. Year 6 <ul style="list-style-type: none"> Take measurements, using a range of scientific equipment, with increasing accuracy and precision, taking repeat readings when appropriate. Aim:	Observing and Measuring LEARNING INTENTION: Year 5 To know that the speed of a motor can be increased and decreased. Year 6 To understand and explain that the speed of a motor can be increased and decreased. Skills: Disciplinary Knowledge: Year 5 <ul style="list-style-type: none"> Take measurements, using a range of scientific equipment, with increasing accuracy and precision. Year 6 <ul style="list-style-type: none"> Take measurements, using a range of scientific equipment, with increasing accuracy and precision, taking repeat readings when appropriate. Aim: Develop scientific knowledge and conceptual understanding through the specific disciplines of physics.

	Develop scientific knowledge and conceptual understanding through the specific disciplines of physics.	
Key Vocabulary: switch, open, closed, circuit, current, flow, travel	Key Vocabulary: current, volt, voltage, brightness, bulb, cell , electrons, electrical energy.	Key Vocabulary: speed, motor, increase, decrease , electric current, slower, faster
Key Knowledge: Child: <ul style="list-style-type: none"> When a switch is closed, it completes the circuit and allows a current to flow all the way around it. When a switch is open, it creates a gap and the current cannot travel around the circuit. Teacher:	Key Knowledge: Child: <ul style="list-style-type: none"> The higher the voltage, the higher is the current. The higher the current, the higher the brightness. The more voltage flowing through a lamp, buzzer or motor, the brighter the lamp, the louder the buzzer and the faster the motor. Teacher: <ul style="list-style-type: none"> Voltage is measured in volts (V) and is a measure of the difference in electrical energy between two parts of a circuit. The bigger the voltage, the more electrons are pushed through the circuit. 	Key Knowledge: Child: <ul style="list-style-type: none"> The speed of a motor can be increased and decreased by changing the electric current. Teacher: <ul style="list-style-type: none"> A small current means a slower speed. A large current means a faster speed.
Assessment Cumulative quiz. Retrieval practice.		